



# UNIVERSITY OF MINES AND TECHNOLOGY, TARKWA

## FIRST SEMESTER EXAMINATIONS, NOV. / DEC. 2018

COURSE NO: GL 233

COURSE NAME: BASIC ELECTRICITY

CLASS: GD II [Unihubgh.com](http://Unihubgh.com)

TIME: 3 HOURS

Name: \_\_\_\_\_ Index Number: \_\_\_\_\_

**Instructions:** Attempt ALL questions in Section A and any Two questions from Section B.

### SECTION A

*This section comprises of 60 multiple-choice questions. Attempt all questions in this section. All questions carry equal marks. Provide your answers on the answer sheets by writing the alphabet corresponding to the correct answer in each question.*


- The algebraic sum of the current entering a node at any instant is equal to
  - the algebraic sum of the current leaving the node
  - sum of the current any point
  - zero
  - sum of current flowing into the node
- A battery of emf 12 V and internal resistance  $1.5 \Omega$  is required to give a current of 0.60 A when connected to an external load of resistance, R. calculate the value of R.
  - $4.8 \Omega$
  - $18.5 \Omega$
  - $20.0 \Omega$
  - $21.5 \Omega$
- A 6.00-V battery is connected to a parallel combination of two resistors, whose values are  $8.0 \Omega$  and  $12.0 \Omega$ . What is the total power (in watts) dissipated?
  - 0.30
  - 3.00
  - 4.50
  - 7.50
- Thevenin's theorem converts a circuit to an equivalent form consisting of
  - a current source in series with a resistor
  - a current source in parallel with a resistor
  - a voltage source in series with a resistor
  - a voltage source in parallel with a resistor
- Norton's theorem is valid for network containing only
  - resistance
  - reactance
  - linear elements
  - no linear elements
- A certain series circuit has  $50 \Omega$ ,  $100 \Omega$  and  $120 \Omega$  resistors in series. If the  $50 \Omega$  resistor is removed, the current will
  - become zero
  - will increase





28. A capacitor  $C$  has a charge  $Q$ . the actual charges on its plates are
- $Q, 0$
  - $Q/2, Q/2$
  - $Q, Q$
  - $Q, -Q$
29. Doubling the voltage across a given capacitor causes the energy stored in that capacitor to
- reduce to one half
  - double
  - quadruple
  - reduce to one fourth
30. The capacitance of a parallel plate capacitor is
- proportional to the plate area
  - inversely proportional to the plate area
  - proportional to the charge stored
  - proportional to the plate separation
31. A parallel plate capacitor has plates each of area  $0.01\text{m}^2$  and with separation  $0.25\text{ mm}$ . What is its capacitance in free space?
- $40\text{ nF}$
  - $0.35\text{ nF}$
  - $4.4\text{ }\mu\text{F}$
  - $88\text{ pF}$
32. Let  $Q$  denote charge,  $V$  denote potential difference and  $E$  denote stored energy. Of these quantities, capacitors in series must have the same:
- $Q$  only
  - $V$  only
  - $E$  only
  - $Q$  and  $E$  only
33. A charge of  $1.5\text{ }\mu\text{C}$  is carried on 2 parallel rectangular plates each measuring  $60\text{ mm}$  by  $80\text{ mm}$ . If the plates are spaced  $10\text{ mm}$  apart and the voltage between them is  $0.5\text{ kV}$ , then the electric field strength is
- $312.5\text{ }\mu\text{C}/\text{m}^2$
  - $50\text{ kV}$
  - $4.5\text{ V}/\text{m}$
  - $50\text{ 000 V}/\text{m}$
34. How many plates has a parallel plate capacitor having a capacitance of  $5\text{ nF}$ , if each plate is  $40\text{ mm}$  by  $40\text{ mm}$ , and each dielectric is  $0.102\text{ mm}$  thick with a relative permittivity of  $6$ ?
- $7$
  - $8$
  - $10$
  - $12$
35. A  $3300\text{ pF}$  capacitor is required to store  $0.5\text{ mJ}$  of energy. The potential difference to which the capacitor must be charged is
- $220\text{ V}$
  - $0.300\text{ kV}$
  - $0.23\text{ kV}$
  - $550\text{ V}$
36. Two capacitors having capacitances of  $10\text{ }\mu\text{F}$  and  $15\text{ }\mu\text{F}$  are connected in series. The value of a third capacitor when connected in series with the other two giving a resultant capacitance of  $3\text{ }\mu\text{F}$  will be
- $6\text{ }\mu\text{F}$
  - $9\text{ }\mu\text{F}$
  - $28\text{ }\mu\text{F}$
  - $36\text{ }\mu\text{F}$

Use Figure 1 to answer questions 37 to 40.

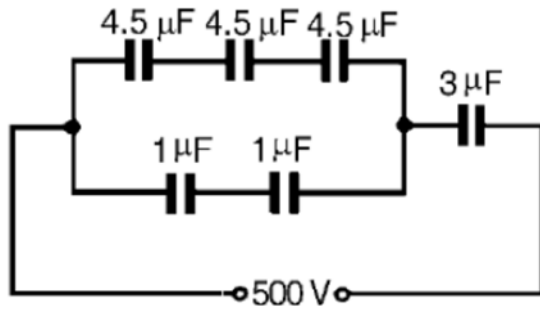

**Figure 1** for questions 37 to 40

37. Find the equivalent circuit capacitance.

- a.  $1.2 \mu F$
- b.  $1.5 \mu F$
- c.  $3 \mu F$
- d.  $47 \mu F$

38. What is the voltage across the  $3 \mu F$  capacitor?

- a. 100 V
- b. 200 V
- c. 300 V
- d. 500 V

39. Determine the charge on a  $1 \mu F$  capacitor.

- a.  $600 \mu C$
- b.  $450 \mu C$
- c.  $150 \mu C$
- d.  $100 \mu C$

40. Find the voltage across a  $4.5 \mu F$  capacitor

- a. 100 V
- b. 200 V
- c. 300 V
- d. 500 V

41. A soft iron bar is introduced inside a current carrying solenoid. The magnetic field inside the solenoid

- a. will become zero
- b. will decrease
- c. will increase
- d. will remain unaffected

42. The direction of the force on a current-carrying wire placed in a magnetic field depends on

- a. the direction of the current
- b. the direction of the field
- c. the direction of current as well as field
- d. none of these

43. Electromagnetic induction is the

- a. charging of a body with a positive charge
- b. production of current by relative motion between a magnet and a coil
- c. rotation of the coil of an electric motor
- d. generation of magnetic field due to a current carrying solenoid

44. In case of two circuits, the magnetic flux linked with one due to a unit current flowing in the other is called
- induced current
  - induced emf
  - self-inductance of the first circuit
  - mutual inductance of the two circuits
45. A material that can be permanently magnetized is generally said to be
- magnetic
  - electro magnetic
  - permanently magnetic
  - ferromagnetic
46. Lines of magnetic flux are said to originate
- in atoms of ferromagnetic materials
  - at a north magnetic pole
  - where the lines converge to a point
  - in charge carriers
47. The magnetic flux around a straight, current-carrying wire
- gets stronger with increasing distance from the wire
  - is strongest near the wire
  - does not vary in strength with distance from the wire
  - consists of straight lines parallel to the wire
48. If a wire coils has 10 turns and carries 500 mA of current, what is the magnetomotive ampere-turns.
- 0.02
  - 5.0
  - 50
  - 5000
49. The flux density (T) existing in an area of  $400 \text{ mm}^2$  if a uniform magnetic flux of  $300 \mu\text{Wb}$  exists at right angles to that area is
- 0.22
  - 0.75
  - 1.33
  - 1.85
50. The flux density (T) produced in an iron ring of relative permeability 1600 which is uniformly wound with a coil producing a magnetic field strength of 500 A/m is given as
- 5.21
  - 2.05
  - 1.01
  - 0.45
51. A current-carrying conductor is situated at right-angles in a uniform magnetic field having a density of 0.3 T. The force in newtons per length on the conductor when the current is 200 A is
- 30
  - 60
  - 100
  - 600
52. A coil of 200 turns is wound uniformly over a wooden ring having a mean circumference of 600 mm and a uniform cross-sectional area of  $500 \text{ mm}^2$ . If the current through the coil is 4 A, the flux density will be

- a.  $1675 \mu T$
- b.  $1333 T$
- c.  $160 T$
- d.  $0.7 \mu T$

53. The difference between alternating (ac) and direct current (dc) is

- a. ac changes value but dc does not
- b. ac changes direction and dc does not
- c. both ac and dc change value and direction
- d. both (a) and (b)

54. The number of cycles completed in one second is called

- a. frequency
- b. period
- c. peak voltage
- d. amplitude

55. When a sine wave has a frequency of 80 Hz, in 5 seconds it goes through \_\_\_\_\_ cycles.

- a. 1/16
- b. 16
- c. 80
- d. 400

56. If the peak value of a sine wave is 10 V, the peak-to-peak value is \_\_\_\_\_ volts

- a. 5
- b. 10
- c. 20
- d. 100


57. What is the instantaneous peak voltage at  $250^\circ$  on a 6 V peak sine wave?

- a. -26.13 V
- b. -5.64 V
- c. +5.64
- d. +26.13

58. The rms value of the ac voltage  $v(t) = 314 \sin 200t$  is

- a. 141.42 V
- b. 157.23 V
- c. 200 V
- d. 314 V

59. The phase angle between the two waveforms in the given circuit equals \_\_\_\_\_

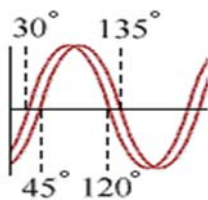

**Figure 2** for question 59

- a.  $15^\circ$
- b.  $45^\circ$
- c.  $75^\circ$
- d.  $255^\circ$


60. If the rms current through a  $10 \text{ k}\Omega$  resistor is 5 mA, the rms voltage drop across the resistor \_\_\_\_\_ volts

- a. 5
- b. 7.07
- c. 70.7
- d. 50

## SECTION B

### Question 1


- (a) Differentiate between
- i. active and passive element
  - ii. conductance and conductivity
- (4 marks)
- (b) Using Thevenin's theorem, determine the current in the  $8\text{-}\Omega$  resistor in Figure 3

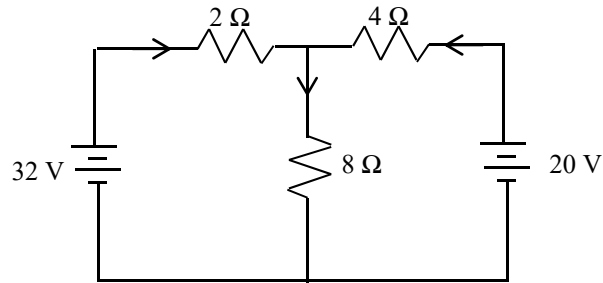

**Figure 3** for question 1(b)

(12 marks)

- (c) Use the principle of superposition to find the current  $I_{10}$  in the network shown in Figure 4.

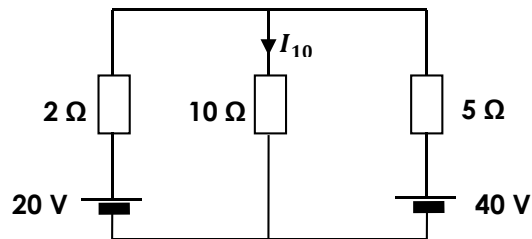

**Figure 4** for question 1(c)

(14 marks)

### Question 2

- (a) Define the following terms as applied to electrostatics
- i. Electric field
  - ii. Electric flux
  - iii. Electric field strength
- (6 marks)
- (b) An alternating current of frequency 50 Hz has a maximum value of 100 A.
- i. Write down an expression for the instantaneous current  $i$
  - ii. Determine the *period* and the *rms* value,  $I_{rms}$
  - iii. Find the value of the current  $\frac{1}{600}$  second after the current is zero.
- (9 marks)
- (c) A parallel-plate capacitor has plate area of  $100\text{ cm}^2$  and a separation of 2.5 mm. A potential difference of 1.0 kV is applied across the plates with only air between the plates. The battery is then disconnected, and a piece of glass ( $\epsilon_r = 8.0$ ) is inserted to completely fill the space between the plates.
- ( $\alpha$ ) What is the

- i. Capacitance
  - ii. Charge on the plates and
  - iii. Electric field intensity **before** the dielectric is inserted?
- ( $\beta$ ) Determine the
- i. Capacitance
  - ii. Charge on the plates
  - iii. Potential difference across the plates
  - iv. Electric flux density and
  - v. Maximum energy stored by the capacitor **after** the dielectric is inserted.
- (15 marks)**


### Question 3

(a) Define the following terms and state their respective units of measurements:

- i. Magnetomotive force
- ii. Magnetic flux
- iii. Reluctance

**(6 marks)**

- (b) Figure 5 shows an iron ring of mean circumference  $40\text{ cm}$  and cross-sectional area  $25\text{ mm}^2$  with a relative permeability of  $800$ . It has a coil of  $100$  turns wound around it and a  $1\text{ mm}$  air gap cut radially through it. Calculate the current in the coil to maintain a flux density of  $0.42\text{ T}$  in the iron ring and in the air gap. **(12 marks)**

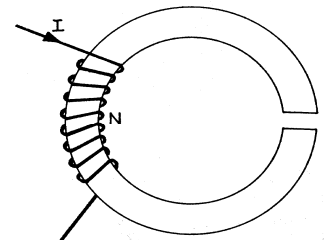

**Figure 5 for question 3 (b)**

- (c) A rectangular shaped core is made of mild-steel plate  $20\text{ mm} \times 30\text{ mm}$  cross-section. The mean length of the magnetic path is  $45\text{ cm}$ . The coil has  $500$  turns and current  $0.8\text{ A}$ . If the relative permeability of mild steel is  $950$ ,

Calculate:

- i. magnetising force
- ii. ampere-turns required
- iii. flux density
- iv. reluctance
- v. flux of magnetic circuit

**Examiners: S. Ofori/ Dr J. C. Attachie**