



**UNIVERSITY OF MINES AND TECHNOLOGY, TARKWA**  
**FIRST SEMESTER EXAMINATIONS, NOV/DEC 2018**


**COURSE NO:** EL 471  
**COURSE NAME:** Power Systems Protection and Control  
**CLASS:** EL IV **TIME:** 3 Hours

Name: \_\_\_\_\_ Index Number: \_\_\_\_\_

**INSTRUCTION: ATTEMPT ALL**  
**QUESTIONS IN THE ANSWER BOOKLET PROVIDED**

**QUESTION 1**

- (a) Sketch an **approximate equivalent circuit diagram** of a current transformer. (5 mks)
- (b) Evaluate the performance of the multiratio CT in Figure 1 with a 100:5 CT ratio, for the following secondary output currents ( $I_s$ ) and burdens ( $Z_B$ ):
- (i)  $I_s = 5$  A and  $Z_B = 0.5 \Omega$ ;
  - (ii)  $I_s = 8$  A and  $Z_B = 0.8 \Omega$ ; and
  - (iii)  $I_s = 15$  A and  $Z_B = 1.5 \Omega$ .
- Also, compute the CT error for each output current. (8 mks)

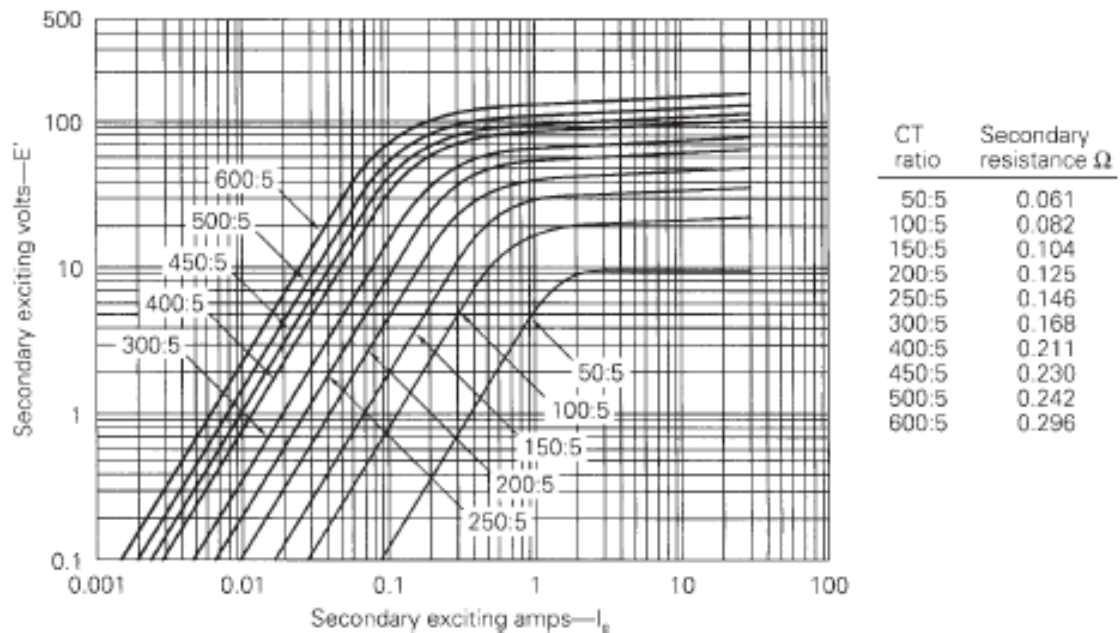

**Figure 1 Excitation Curves for a Multiratio Bushing CT with A C100 ANSI Accuracy Classification**

- (c) Sketch the inverse-time characteristics of an induction disc overcurrent relay. (2 mks)


- (d) Sketch a diagram of the voltage balance differential relay. (2 mks)

**QUESTION 2**

- (a) State and explain briefly any **FOUR** qualities of a protection system. (4 mks)
- (b) Explain using appropriate diagrams the term “protection coordination. (9 mks)
- (c) Give the classifications of relays according to:  
 (i) construction.  
 (ii) application.  
 (iii) characteristics. (9 mks)
- (d) Describe any one method employed for the protection of bus bars. (5 mks)
- (e) Describe with the aid of an appropriate diagram the Merz price system used for the protection of three-phase transmission lines. (6 mks)

**QUESTION 3**

- (a) (i) All the functions and characteristics available with electromechanical relays can be performed by *solid-state devices (relays)*, either as discrete components or as integrated circuits. Explain the term in italics.
- (ii) Mention **THREE** advantages of the solid-state relays. (7 mks)
- (b) Using appropriate diagrams, differentiate between magnitude comparison relaying and phase angle comparison relaying. (10 mks)
- (c) Consider a  $\Delta/Y$ -connected, 20 MVA, 33/11 kV transformer with differential protection applied, for the current transformer ratios shown in Figure 2. Calculate the relay currents on full load. Find the minimum relay current setting to allow 125% overload. (7 mks)

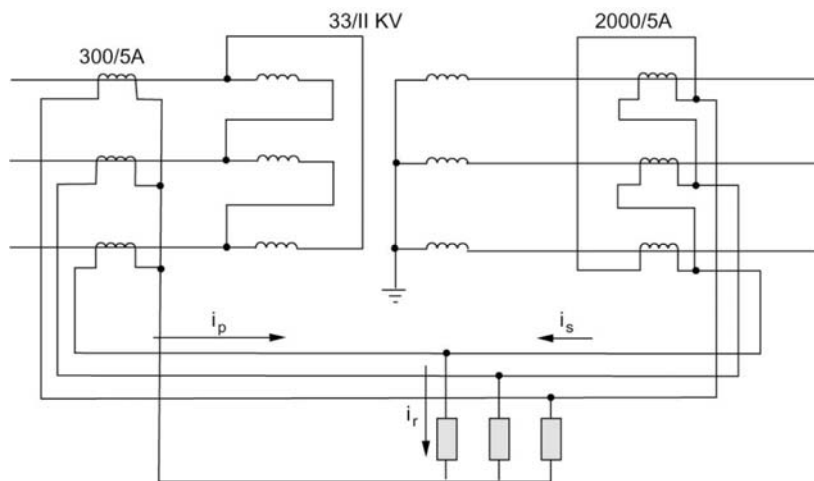

**Figure 2 Differential Protection of a  $\Delta/Y$  Transformer**

**QUESTION 4**

- (a) State **TWO** objectives of power system protection. **(2 mks)**
- (b) Mention **FIVE** causes and **FIVE** undesirable effects of short-circuit faults. **(10 mks)**
- (c) Give the classification of relays based on the following:
- (i) general function.
  - (ii) construction.
  - (iii) incoming signal.
  - (iv) type of protection. **(8 mks)**
- (d) An electromagnetic relay of attracted armature type has constants  $k_1 = 0.6$  and  $k_2 = 10$  find whether the relay will operate or not when:
- (i) A current of 4 A flows through the relay winding.
  - (ii) A current of 5 A flows through the relay winding.
  - (iii) Find the minimum current required to operate the relay. **(6 mks)**

