



UNIVERSITY OF MINES AND TECHNOLOGY, TARKWA
SECOND SEMESTER EXAMINATIONS, APRIL/MAY 2019

COURSE NO: EL 174
COURSE NAME: Semiconductor Devices
CLASS: EL I

TIME: 3 hours

Name: _____

Index Number: _____

Instructions

Attempt all questions in Section A and Question 1 and any other question in Section B.

[Hint: $h = 6.625 \times 10^{-34}$ Js; $m = 9.11 \times 10^{-31}$ kg; $c = 3 \times 10^8$ m/s; $e = 1.6 \times 10^{-19}$ C; $\epsilon_0 = 8.85 \times 10^{-12}$ F/m]

SECTION A

This section comprises of 80 multiple choice questions. Attempt all questions in this section. All questions carry equal marks. Provide your answers in the Answer Booklet by writing the alphabet corresponding to the correct answer in each question.

Atomic Theory

1. According to Bohr's theory of atom, an electron can move in an orbit of _____.
A. any radius
B. certain radius
C. some range of radii
D. none of the above
2. The total energy of a revolving electron in an atom can _____.
A. have any value above zero
B. never be positive
C. never be negative
D. not be calculated
3. An atom is said to be ionised when any one of its orbiting electron _____.
A. jumps from one orbit to another
B. is raised to a higher orbit
C. comes to the ground state
D. is completely removed
4. Which subatomic particles have opposite charges?
A. Electrons and neutrons
B. Energy and neutrons
C. Protons and electrons
D. Protons and neutrons
5. Which subatomic particles have the same relative mass?
A. Electrons and protons
B. Energy and protons
C. Neutrons and electrons
D. Protons and neutrons

Semiconductor Physics

6. A semiconductor is formed by _____ bonds.
A. covalent
B. electrovalent
C. co-ordinate
D. none of the above
7. The most commonly used semiconductor is _____.
A. germanium
B. silicon
C. carbon
D. sulphur

20. Consider an x-ray with a wavelength of $\lambda = 0.708 \times 10^{-8}$ cm. Calculate the photon energy corresponding to this wavelength.
- A. 1.75×10^4 eV
 B. 2.81×10^{-8} eV
 C. 2.81×10^{-15} eV
 D. 7.08×10^4 eV
21. Consider an electron traveling at a velocity of 10^7 cm/s. Calculate its de Broglie wavelength.
- A. 72.7 Å
 B. 7.27 Å
 C. 0.727 Å
 D. 9.11 Å

Diodes and Diode Applications

22. In the breakdown region, a zener diode behaves like a _____ source.
- A. constant voltage
 B. constant current
 C. constant resistance
 D. none of the above
23. A zener diode is destroyed if it _____.
- A. is forward biased
 B. is reverse biased
 C. carrier more than rated current
 D. none of the above
24. A series resistance is connected in the zener circuit to _____.
- A. properly reverse bias the Zener
 B. protect the Zener
 C. properly forward bias the Zener
 D. none of the above
25. A zener diode is _____ device.
- A. a non-linear
 B. a linear
 C. an amplifying
 D. none of the above
26. A zener diode has _____ breakdown voltage.
- A. undefined
 B. sharp
 C. zero
 D. none of the above
27. _____ rectifier has the lowest forward resistance.
- A. solid state
 B. vacuum tube
 C. gas tube
 D. none of the above
28. Mains ac power is converted into dc power for _____.
- A. lighting purposes
 B. heaters
 C. using in electronic equipment
 D. none of the above
29. The disadvantage of a half-wave rectifier is that the _____.
- A. components are expensive
 B. diodes must have a higher power rating
 C. output is difficult to filter
 D. none of the above
30. If the ac input to a half-wave rectifier is an rms value of $400/\sqrt{2}$ volts, then diode PIV rating is _____.
- A. $400/\sqrt{2}$ V
 B. 400 V
 C. $400\sqrt{2}$ V
 D. none of the above
31. The ripple factor of a half-wave rectifier is _____.
- A. 2
 B. 1.21
 C. 2.5
 D. 0.48
32. There is a need of transformer for _____.
- A. half-wave rectifier
 B. centre-tap full-wave rectifier
 C. bridge full-wave rectifier
 D. none of the above

58. What is the collector current for a CE configuration with a beta of 100 and a base current of $30\ \mu\text{A}$?
- A. $30\ \mu\text{A}$
 - B. $0.3\ \mu\text{A}$
 - C. $3\ \text{mA}$
 - D. $3\ \text{MA}$

Field Effect Transistors

59. A JFET has three terminals, namely _____.
- A. cathode, anode, grid
 - B. emitter, base, collector
 - C. source, gate, drain
 - D. none of the above
60. A JFET is also called _____ transistor.
- A. unipolar
 - B. bipolar
 - C. unijunction
 - D. none of the above
61. A JFET has high input impedance because _____.
- A. it is made of semiconductor material
 - B. input is reverse biased
 - C. of impurity atoms
 - D. none of the above
62. In a JFET, I_{DSS} is known as _____.
- A. drain to source current
 - B. drain to source current with gate shorted
 - C. drain to source current with gate open
 - D. none of the above
63. A MOSFET is sometimes called _____ JFET.
- A. many gate
 - B. open gate
 - C. insulated gate
 - D. shorted gate
64. A MOSFET uses the electric field of a _____ to control the channel current.
- A. capacitor
 - B. battery
 - C. generator
 - D. none of the above
65. The pinch-off voltage in a JFET is analogous to _____ voltage in a vacuum tube.
- A. anode
 - B. cathode
 - C. grid cut off
 - D. none of the above
66. A MOSFET differs from a JFET mainly because _____.
- A. of power rating
 - B. the MOSFET has two gates
 - C. the JFET has a pn junction
 - D. none of above
67. A certain D-MOSFET is biased at $V_{\text{GS}} = 0\ \text{V}$. Its datasheet specifies $I_{\text{DSS}} = 20\ \text{mA}$ and $V_{\text{GS(off)}} = -5\ \text{V}$. The value of the drain current is _____.
- A. $20\ \text{mA}$
 - B. $0\ \text{mA}$
 - C. $40\ \text{mA}$
 - D. $10\ \text{mA}$
68. A certain p-channel E-MOSFET has a $V_{\text{GS(th)}} = -2\ \text{V}$. If $V_{\text{GS}} = 0\ \text{V}$, the drain current is _____.
- A. $0\ \text{mA}$
 - B. $I_{\text{D(on)}}$
 - B. maximum
 - D. I_{DSS}

Silicon Controlled Rectifiers

69. Which of the following devices does not have a cathode terminal?
A. SCR
B. SCS
C. Triac
D. Shockley diode
70. Which of the following devices is unquestionably of the greatest interest today?
A. SCR
B. GTO
C. LASCR
D. SCS
71. Which of the following devices has a negative-resistance region in its characteristics curve?
A. SCR
B. SCS
C. Unijunction transistor
D. Phototransistor
72. Which one of the SCR terminals fires the SCR?
A. Anode
B. Cathode
C. Gate
D. All of the above
73. Which of the following devices has the smallest turn-off time?
A. SCR
B. GTO
C. SCS
D. LASCR
74. Which of the following devices has nearly the same turn-on time as turn-off time?
A. SCR
B. GTO
C. SCS
D. LASCR
75. Which of the transistors of an SCR are conducting when the SCR is fired and is in the conduction mode?
A. npn
B. pnp
C. Both npn and pnp
D. Neither npn nor pnp
76. Which of the following devices has (have) four layers of semiconductor materials?
A. SCS
B. GTO
C. LASCR
D. All of the above
77. Which of the following parameters are usually provided by the manufacturer on the specification sheet for SCRs?
A. Turn-on time (t_{on})
B. Turn-off time (t_{off})
C. Junction and case temperatures (t_j and t_c)
D. All of the above
78. Which of the following areas is (are) applications of an SCS?
A. Counters
B. Pulse generators
C. Voltage sensors
D. All of the above
79. Which of the following is (are) the advantages of the SCS over a corresponding SCR?
A. Reduced turn-off time
B. Increased control and triggering sensitivity
C. More predictable firing situation
D. All of the above
80. Which of the following transistors is an SCR composed of?
A. npn, pnp
B. npn, npn
C. pnp, pnp
D. None of the above













SECTION B

Attempt only two question in this section. Question 1 is compulsory. All questions carry equal marks.

QUESTION 1

- a. Draw the electrical symbol for the following semiconductor devices: zener diode, Schottky diode, tunnel diode, PNP transistor, *n*-channel JFET, *p*-channel D-MOSFET, Dual-gate *n*-channel E-MOSFET, and LASCR. [8 marks]
- b. Identify each of the electronic symbols in Table 1 below. [12 marks]

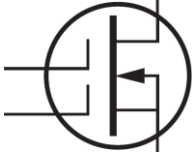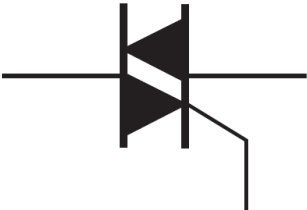Table 1 Electronic symbols

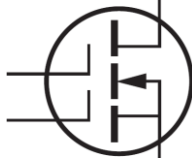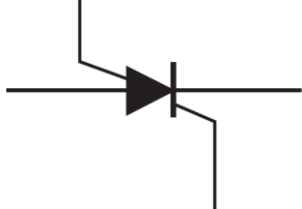SN	CIRCUIT SYMBOL	SN	CIRCUIT SYMBOL	SN	CIRCUIT SYMBOL
a.		b.		c.	
d.		e.		f.	
g.		h.		i.	
j.		k.		l.	

Question 2

- a. Find the value of R_S required to self-bias a *p*-channel JFET with $I_{DSS} = 18 \text{ mA}$ and $V_{GS(off)} = 8 \text{ V}$. Assume V_{GS} to be 4 V . [5 marks]
- b. Graphically determine the Q-point for the circuit in Figure 1(a) using the transfer characteristic curve in Figure 1(b). [5 marks]
- c. The datasheet for an E-MOSFET gives $I_{D(on)} = 100 \text{ mA}$ at $V_{GS} = 8 \text{ V}$ and $V_{GS(th)} = 4 \text{ V}$. Find I_D when $V_{GS} = 6 \text{ V}$. [5 marks]
- d. For a certain D-MOSFET, $I_{DSS} = 18 \text{ mA}$ and $V_{GS(off)} = 10 \text{ V}$.
- Is this an *n*-channel or a *p*-channel? [1 mark]
 - Determine I_D at $V_{GS} = 4 \text{ V}$. [2 marks]
 - Determine I_D at $V_{GS} = -4 \text{ V}$. [2 marks]

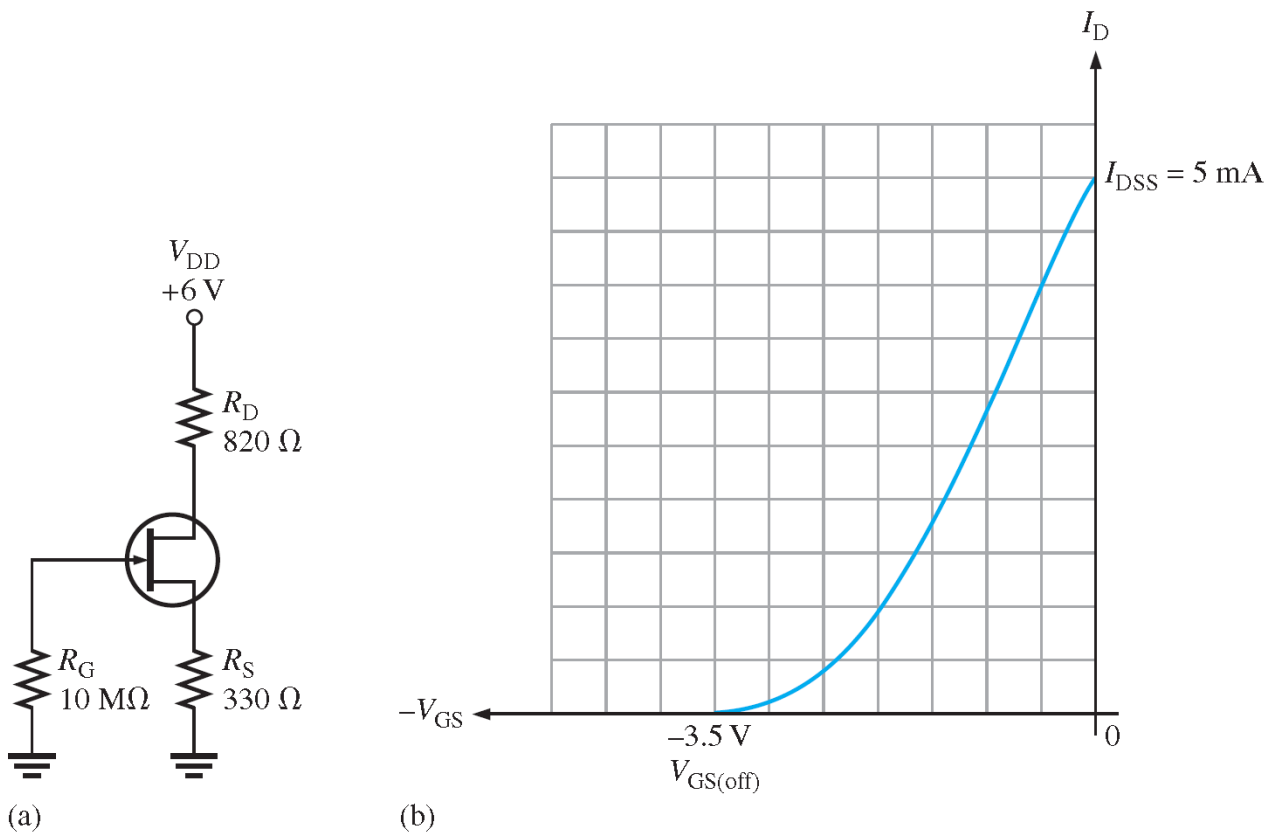


Figure 1 Electric circuit and its corresponding graph for Question 2b

Question 3

- Determine the resistance of a certain 4-layer diode in the forward-blocking region if $V_{AK} = 15 \text{ V}$ and $I_A = 1 \mu\text{A}$. If the forward-breakover voltage is 50 V , how much must V_{AK} be increased to switch the diode into the forward-conduction region? [5 marks]
- Explain the operation of an SCR in terms of its transistor equivalent. [5 marks]
- Explain the turn-on and turn-off operation of an SCS in terms of its transistor equivalent. [5 marks]
- To what value must the variable resistor be adjusted in Figure 2 to turn the SCR off? Assume $I_H = 10 \text{ mA}$ and $V_{AK} = 0.7 \text{ V}$. [5 marks]

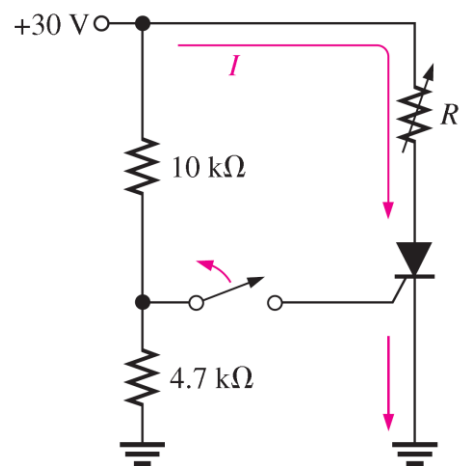


Figure 2 Electric circuit for Question 3d

Dr S. Nunoo/J. C. Attachie